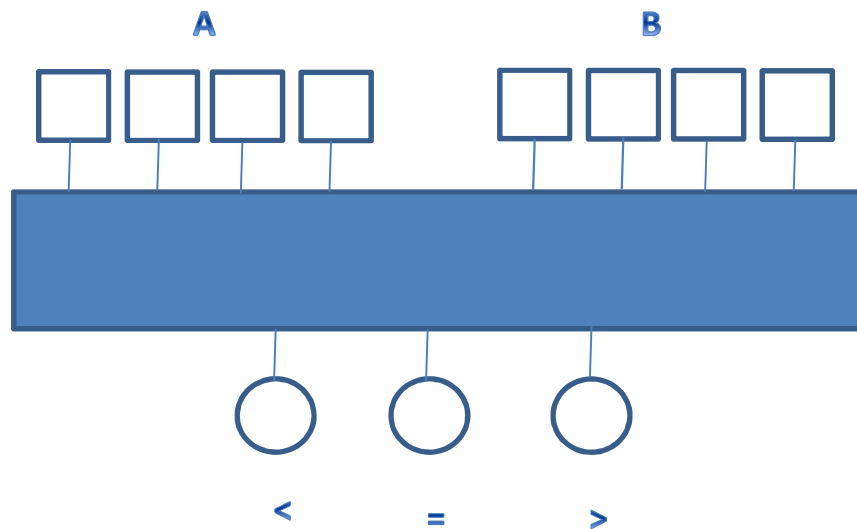


CS240 Spring 2013 Project

2's Complement Comparator

Due: Midnight, April 29, 2013

Create a 4 bit 2's Complement Comparator. The circuit will look like this:



### Inputs:

A – a 4 bit 2's complement number

B – a 4 bit 2's complement number

### Outputs:

One of the three outputs will be set to '1' depending on the input values.

### Requirements:

- 1) You may only use the following built-in LOGISIM gates: AND, OR, XOR, NOT.
- 2) You may NOT use any other prebuilt LOGISIM circuit (i.e. Adder, Multiplexer, etc.), however, you are free to construct your own Adders, Multiplexers, etc. using AND, OR, XOR, NOT gates.

### Submission:

- 1) Name the file: CS240\_Lastname\_Firstname.circ where you will replace the firstname and lastname with your own name.
- 2) TEST your file, preferably on another computer. If it doesn't load, you will get a zero.
- 3) Upload your submission to Blackboard.